
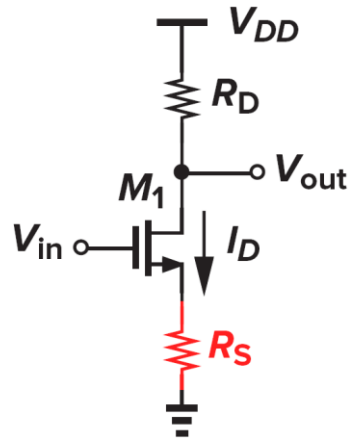


# Common source with source degradation


## Source follower

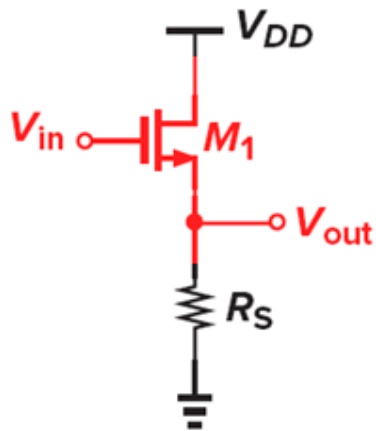

**CS with  
source degradation**




**Source follower**

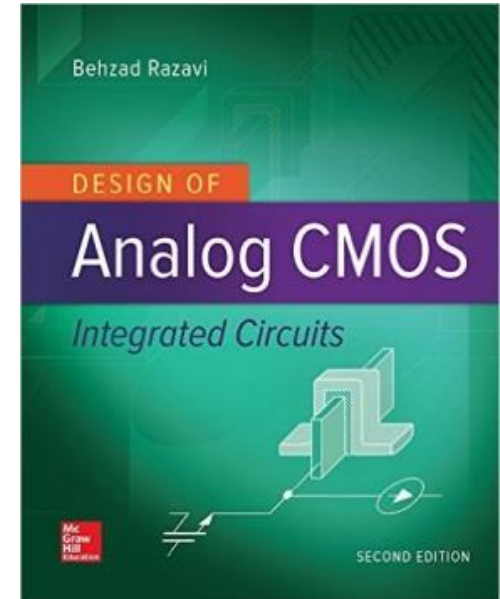

**Behzad Razavi:**  
*Design of Analog Integrated Circuit,*  
McGraw-Hill, 2016

# **Common source with source degradation**



# CS with source degeneration

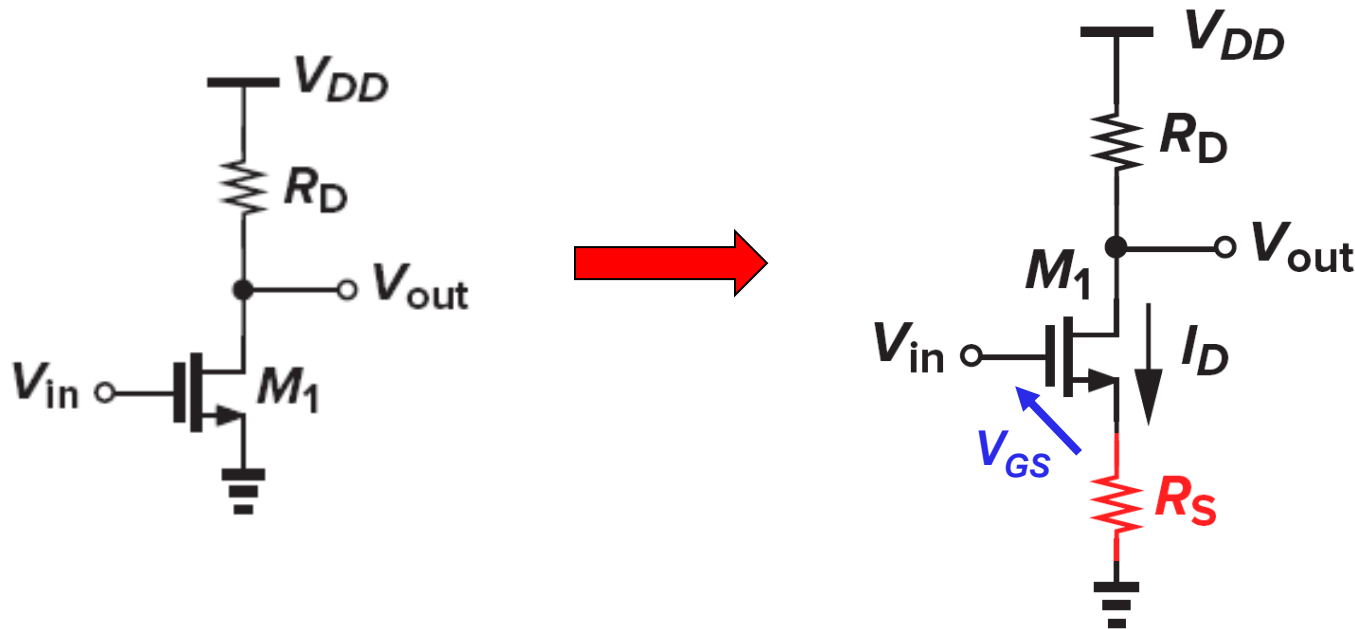

In some applications, the nonlinear dependence of the drain current upon the overdrive voltage introduces excessive nonlinearity, making it desirable to “soften” the device characteristics. As depicted in Fig. (above), this can be accomplished by placing a “**degeneration**” resistor in series with the source terminal so as to make the input device more linear.

Let us neglect channel-length modulation and body effect. Here, as  $V_{in}$  increases, so do  $I_D$  and the voltage drop across  $R_S$ . That is, a fraction of the change in  $V_{in}$  appears across the resistor rather than as the gate-source overdrive, thus leading to a smoother variation of  $I_D$ . From another perspective, we intend to make the gain equation a weaker function of  $g_m$ . Since  $V_{out} = V_{DD} - I_D R_D$ , the nonlinearity of the circuit arises from the nonlinear dependence of  $I_D$  upon  $V_{in}$ . We note that  $\partial V_{out} / \partial V_{in} = -(\partial I_D / \partial V_{in}) R_D$ , and define the equivalent transconductance of the circuit as  $G_m = \partial I_D / \partial V_{in}$ .
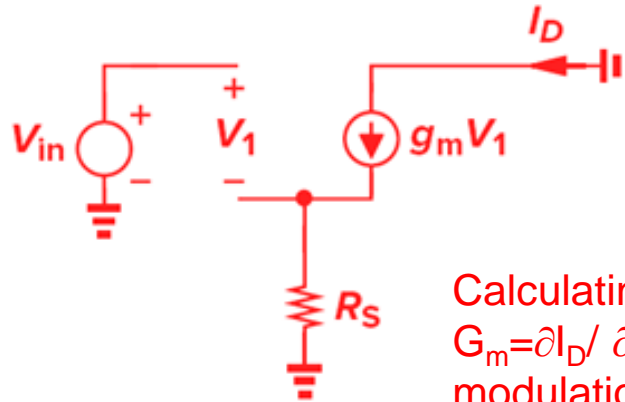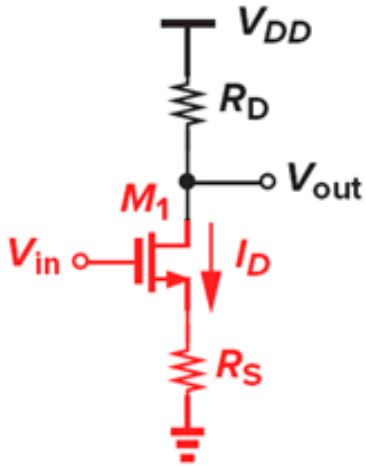
# CS with source degeneration (effective transconductance and gain)



Calculating effective transconductance  
 $G_m = \partial I_D / \partial V_{in}$  neglecting channel length modulation and body effect.

Simple equations for  $G_m$ :

$$V_{in} = V_1 + R_S g_m V_1 \Rightarrow V_{in} = V_1 (1 + g_m R_S)$$

$$I_D = g_m V_1$$

We obtain:

$$I_D / V_{in} = g_m / (1 + g_m R_S)$$

$$G_m = \frac{g_m}{1 + g_m R_S}$$

Small-signal gain:



$$A_v = -G_m R_D$$

$$= \frac{-g_m R_D}{1 + g_m R_S} = -\frac{R_D}{\frac{1}{g_m} + R_S}$$

$$\approx -\frac{R_D}{R_S}$$
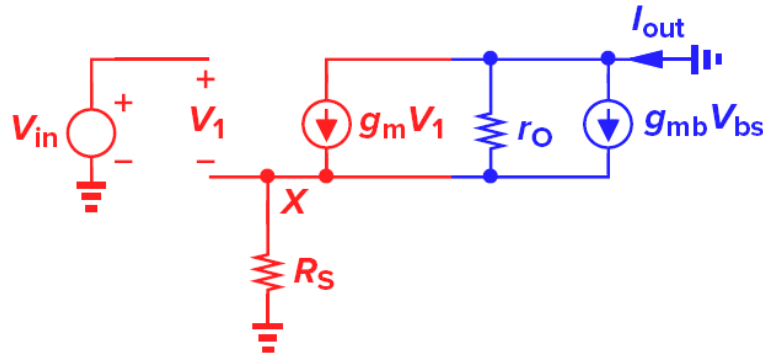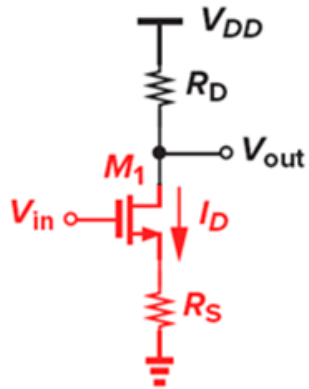
# CS with source degradation

(Homework: effective transconductance with  $r_O$  and  $g_{mb}$ )



Calculating effective transconductance  $G_m$  with channel effect modulation and body effect.

We recognize that:  $V_{in} = V_1 + R_S I_{out}$

It follows that:

$$\begin{aligned} I_{out} &= g_m V_1 - g_{mb} V_X - \frac{I_{out} R_S}{r_O} \\ &= g_m (V_{in} - I_{out} R_S) + g_{mb} (-I_{out} R_S) - \frac{I_{out} R_S}{r_O} \end{aligned}$$

$$\begin{aligned} G_m &= \frac{I_{out}}{V_{in}} \\ &= \frac{g_m r_O}{R_S + [1 + (g_m + g_{mb}) R_S] r_O} \end{aligned}$$

# CS with source degeneration – $R_{out}$



(similar to current source with resistor degeneration)

Another important consequence of source degeneration is the increase in the output resistance of the stage. We calculate the output resistance first with the aid of the equivalent circuit shown in Fig. (below), where the load resistor,  $R_D$ , is excluded for now. Note that body effect is also included to arrive at a general result. Since the current through  $R_S$  is equal to  $I_X$ ,  $V_1 = -I_X R_S$ , and the current flowing through  $r_O$  is given by  $I_X - (g_m + g_{mb})V_1 = I_X + (g_m + g_{mb})R_S I_X$ . Adding the voltage drops across  $r_O$  and  $R_S$ , we obtain:

$$r_O[I_X + (g_m + g_{mb})R_S I_X] + I_X R_S = V_X$$

It follows that:
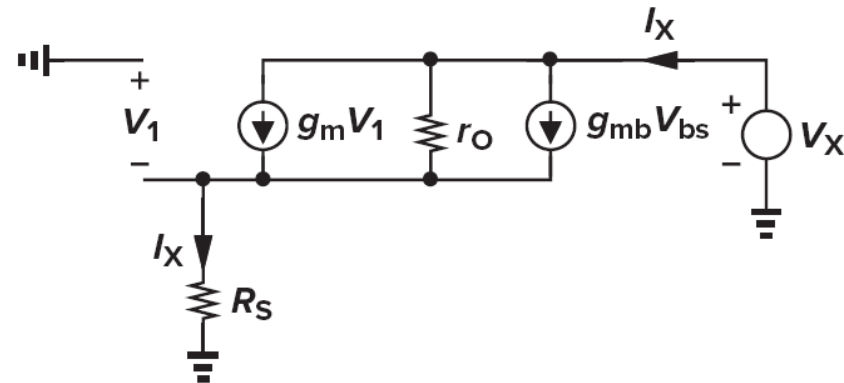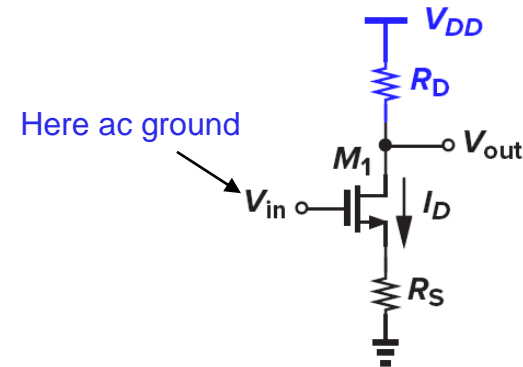
$$\begin{aligned} R_{out} &= [1 + (g_m + g_{mb})R_S]r_O + R_S \\ &= [1 + (g_m + g_{mb})r_O]R_S + r_O \end{aligned}$$



Equation  $R_{out}$  indicates that  $r_O$  is “boosted” by a factor of  $1 + (g_m + g_{mb})R_S$  and then added to  $R_S$ .

As an alternative perspective, eq. suggests that  $R_S$  is boosted by a factor of  $1 + (g_m + g_{mb})r_O$  (a value close to the transistor’s intrinsic gain) and then added to  $r_O$ .

Both views prove useful in analyzing circuits.

# CS with source degradation

( **Homework**: degradation as diode connected MOS)

Assuming  $\lambda = \gamma = 0$ , calculate the small-signal gain of the circuit shown in Fig. 3.28(a).

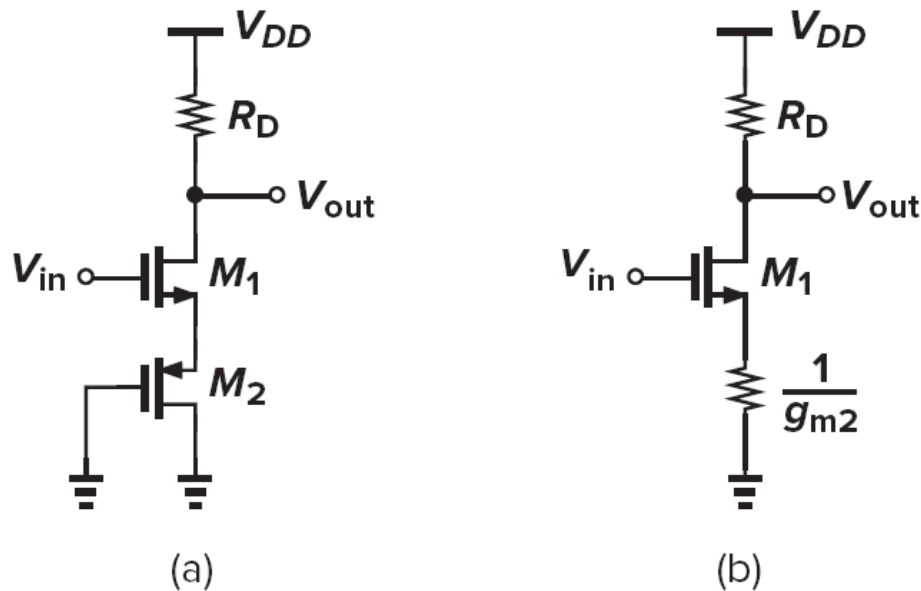


Figure 3.28

## Solution

Noting that  $M_2$  is a diode-connected device and simplifying the circuit to that shown in Fig. 3.28(b), we use the above rule to write


$$A_v = - \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

**Source follower**


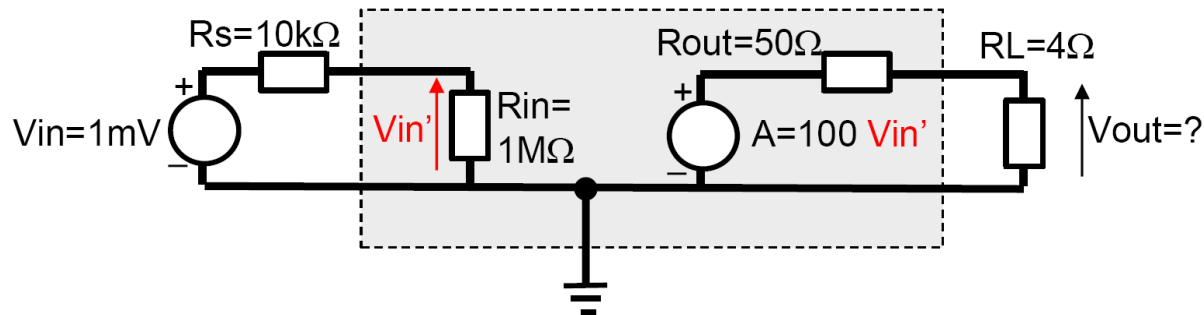
# Voltage buffer (gain = 1V/V, $r_{in}$ – high, $r_{out}$ – small)

**Ex.:**  $V_{in} = 1 \text{ mV}$ ,  $A=100 \text{ V/V}$ ,  $R_s=10\text{k}\Omega$ ,  $R_{in}=1\text{M}\Omega$ ,  $R_{out}=50\Omega$ ,  $R_L=4\Omega$ . Calculate  $V_{out}=?$




$V_{out} = 1 \text{ mV} \times (\text{voltage divider at input}) \times 100\text{V/V} \times (\text{voltage divider at output})$


$V_{out} = 1 \text{ mV} \times (1\text{M}/(10\text{k}+1\text{M})) \times 100\text{V/V} \times (4/(4+50)) = 7.4\text{m}$

**Comment:** It will be better if  $R_{out}$  is small (for voltage amplifier  $R_{out}$  should be small)


**Solution:**

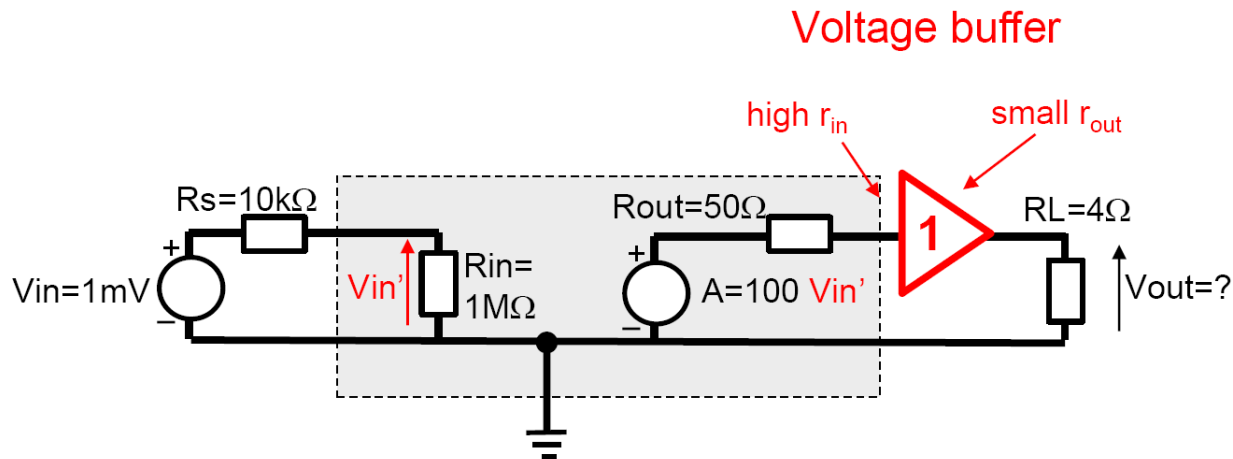

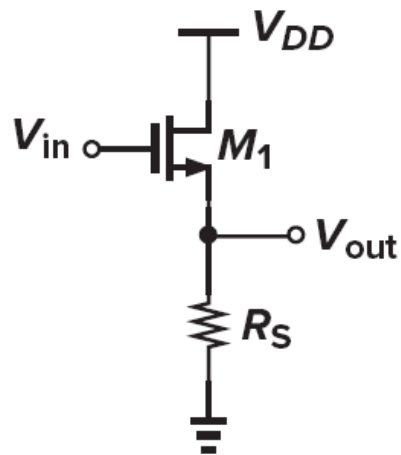
# Common drain = source follower (voltage buffer)



(a)

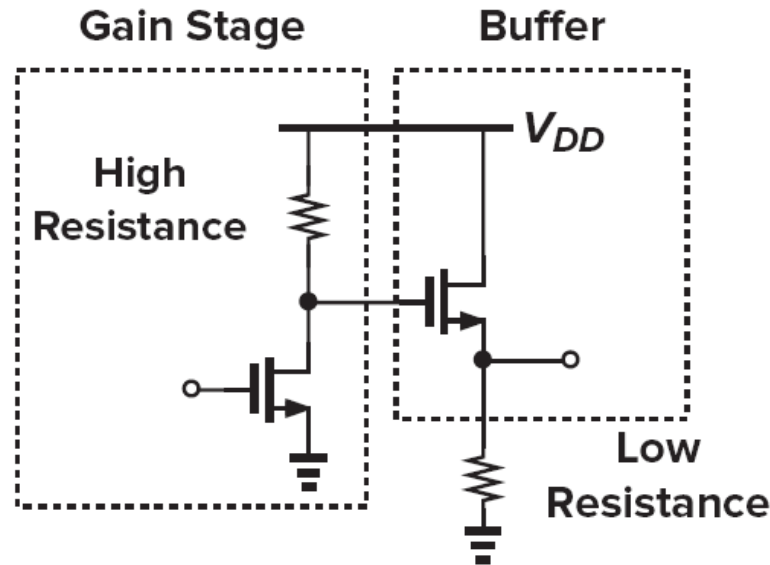

(b)

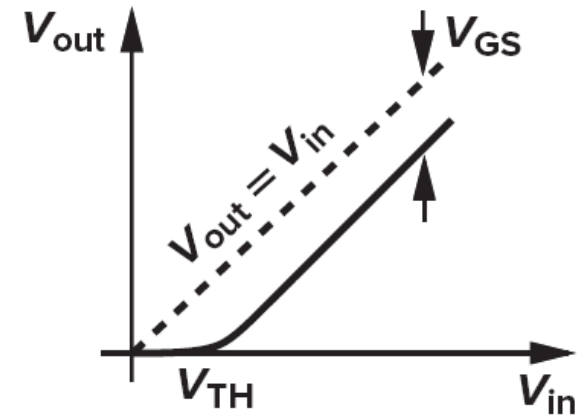


(c)

(a) Source follower, (b) example of its role as a buffer, and (c) its input-output characteristic.
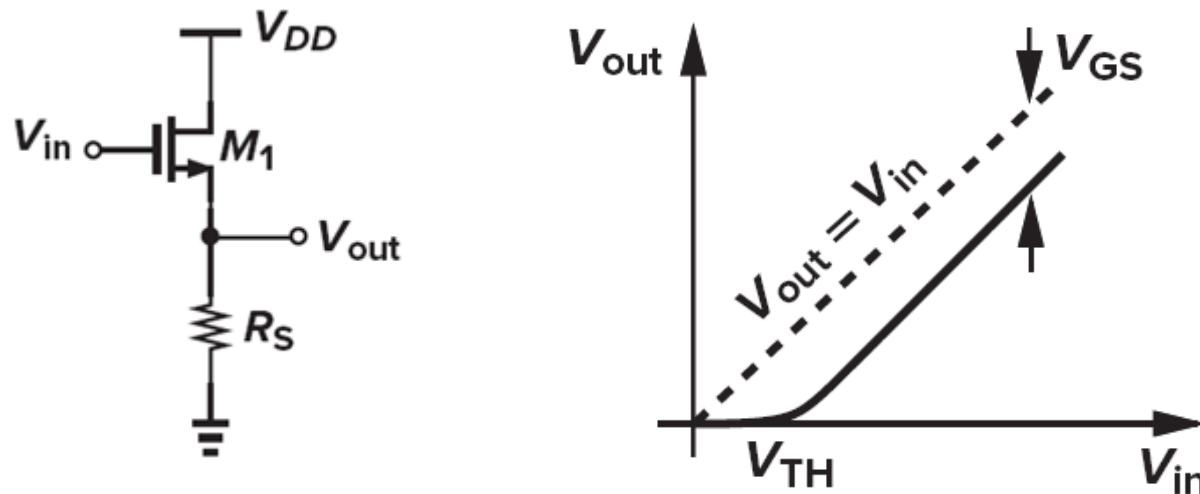
# Source follower

(DC-DC characteristic = large-signal behavior)



Beginning with the large-signal behavior of the source follower, we note that for  $V_{in} < V_{TH}$ ,  $M_1$  is off and  $V_{out} = 0$ . As  $V_{in}$  exceeds  $V_{TH}$ ,  $M_1$  turns on in saturation and  $I_{D1}$  flows through  $R_S$ . As  $V_{in}$  increases further,  $V_{out}$  follows the input with a difference (level shift) equal to  $V_{GS}$ . We can express the input-output characteristic as  $V_{out} = I_D R_S$


$$V_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out})^2 R_S$$

where channel-length modulation is neglected. Let us calculate the small-signal gain of the circuit by differentiating both sides of above eq. with respect to  $V_{in}$  (see next slide) and we obtain:

$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S} \approx \frac{g_m}{g_m + g_{mb}}$$

# Source follower

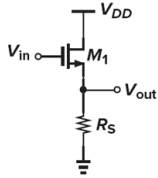**(HOMEWORK: gain calculation from DC-DC characteristic)**



$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out})^2 R_S = V_{out}$$

Let us calculate the small-signal gain of the circuit by differentiating both sides of above eq. with respect to  $V_{in}$ :

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2(V_{in} - V_{TH} - V_{out}) \left( 1 - \frac{\partial V_{TH}}{\partial V_{in}} - \frac{\partial V_{out}}{\partial V_{in}} \right) R_S = \frac{\partial V_{out}}{\partial V_{in}}$$

Since  $\partial V_{TH} / \partial V_{in} = (\partial V_{TH} / \partial V_{SB})(\partial V_{SB} / \partial V_{in}) = \eta \partial V_{out} / \partial V_{in}$ ,

$$\frac{\partial V_{out}}{\partial V_{in}} = \frac{\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out}) R_S}{1 + \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out}) R_S (1 + \eta)}$$




Also, note that

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out})$$

Consequently,

$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$
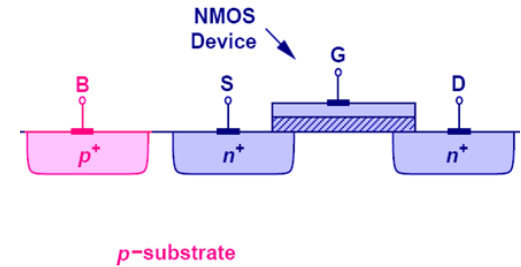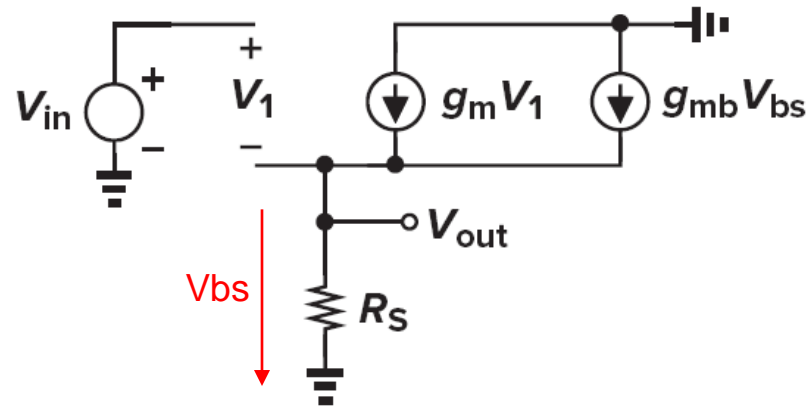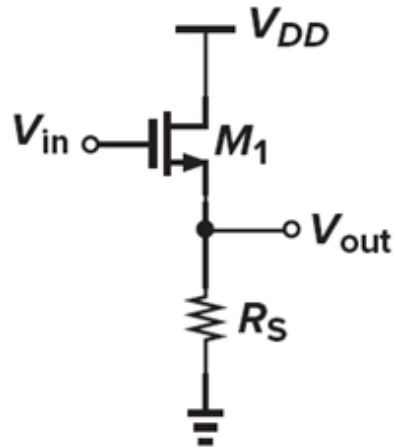
# Source follower biased with current source



NMOS – substrate (bulk) connect to GND

Two simple equation:

$$V_{in} = V_1 + V_{out} \Rightarrow V_1 = V_{in} - V_{out}$$

$$V_{out} = R_S (g_m V_1 + g_{mb} V_{bs})$$


Nothing that:  $V_{out} = -V_{bs}$

We have:

$$V_{out} = R_S (g_m (V_{in} - V_{out}) - g_{mb} V_{out})$$

$$V_{out}/V_{in} = g_m R_S / (1 + (g_m + g_{mb}) R_S)$$


$$A_v \approx \frac{g_m}{g_m + g_{mb}}$$

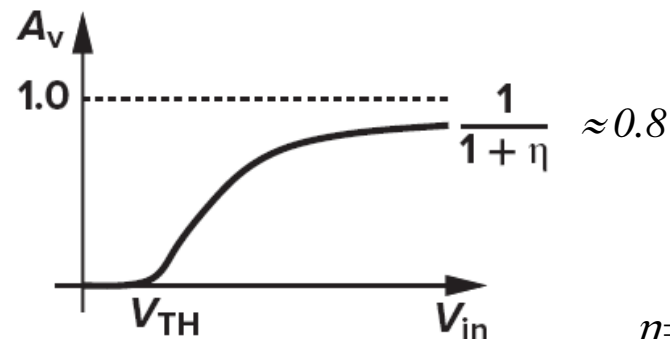

$$\eta = g_{mb}/g_m \approx 0.25$$
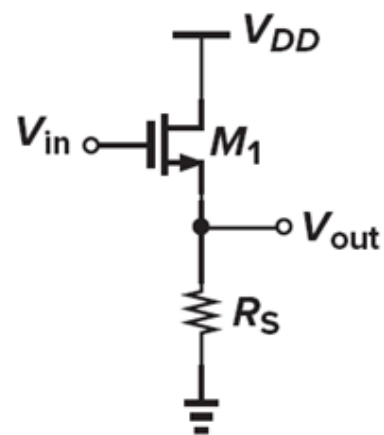
# Source follower



(more easily: gain calculation from small-signal model)



In the source follower of Fig. (left), the drain current of  $M_1$  heavily depends on the input dc level:


$$V_{in} \uparrow \quad I_D \uparrow \quad \text{then} \quad V_{GS} \uparrow$$

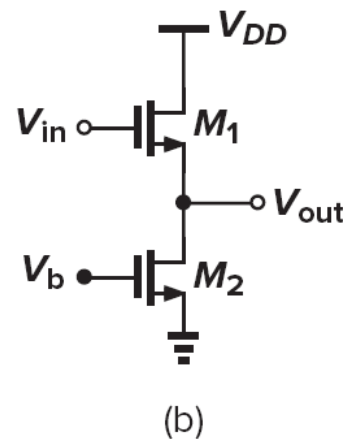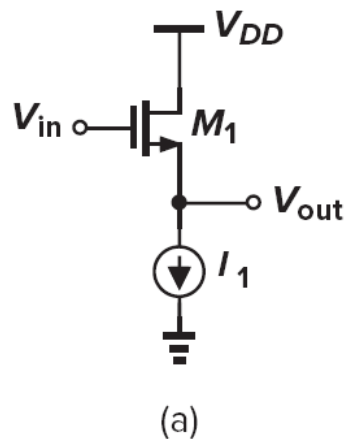means that  $V_{out} = V_{in} - V_{GS}$  does not follow  $V_{in}$  faithfully, thereby incurring **nonlinearity**. To alleviate this issue, the resistor can be replaced by a constant current source as shown in Fig. (bottom). The current source itself is implemented as an NMOS transistor operating in the saturation region.



Source follower using (a) an ideal current source, and (b) an NMOS transistor as a current source.

# Source follower – $R_{out}$

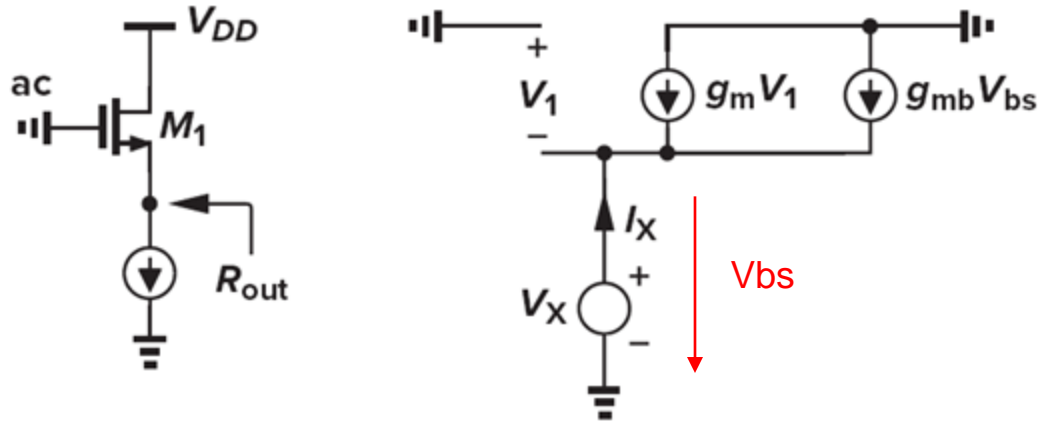


Calculation of the output impedance of a source follower.


Nothing that:  $V_X = -V_{bs} = -V_1$

$$I_X - g_m V_X - g_{mb} V_X = 0 \quad \longrightarrow \quad R_{out} = \frac{1}{g_m + g_{mb}}$$

# Source follower with no body effects

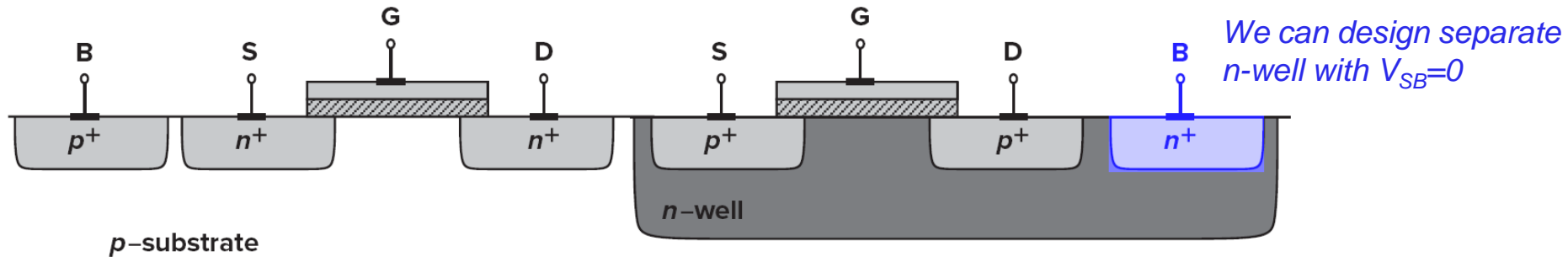


NMOS source follower

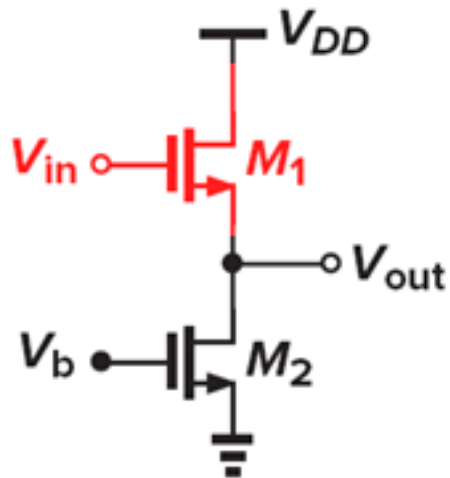

$g_{m1}, g_{mb1}$

$$A_v \approx \frac{g_m}{g_m + g_{mb}}$$

PMOS source follower

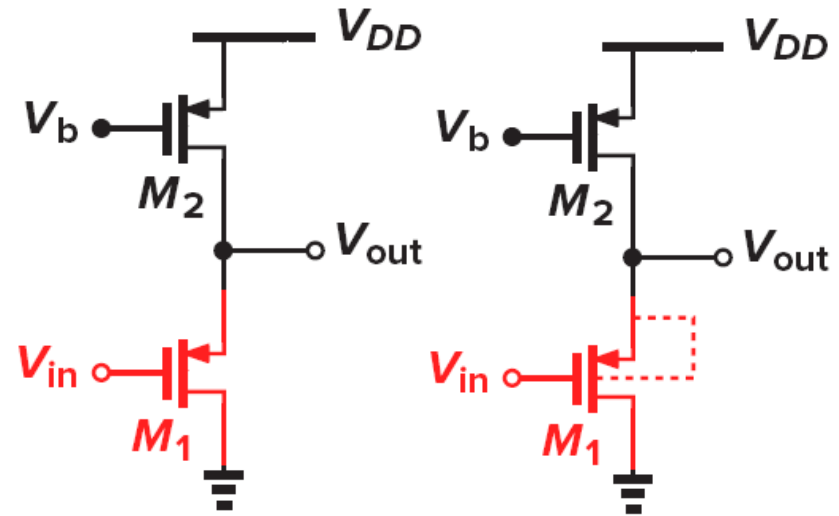

$g_{m1}, g_{mb1}$

$g_{m1}$

$$A_v \approx 1$$