



# FREQUENCY RESPONSE

- **Amplifier Gain vs Frequency**
- **Bode Plots**
- **Association of Poles with Nodes**
- **MOS Intrinsic Capacitances**
- **Transition Frequency of MOS Transistor**
- **Frequency Response of CS Stage**
- **Frequency Response of Source Follower**
- **Frequency Response of CG Stage**
- **Frequency Response of Cascode Stage**
- **Frequency Response of Differential Pairs**

## References

1. B. Razavi, ***Design of Analog CMOS Integrated Circuits***. McGraw-Hill, 2001.
2. B. Razavi, ***Fundamentals of Microelectronics***. Hoboken, NJ: Wiley, 2008.
3. P. Gray, P. Hurst, S. Lewis, R. Meyer, ***Analysis and Design of Analog Integrated Circuits***. Hoboken, NJ: Wiley, 2010.
4. Ali Sheikholeslami, ***Miller's Approximation***. IEEE SSC Magazine, Fall 2015, p.7-8,13
5. W. Sansen, ***Analog Design Essentials***, Springer, 2005

# Amplifier Gain vs Frequency

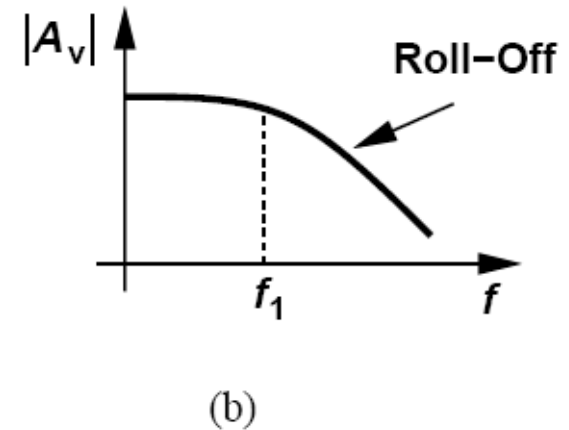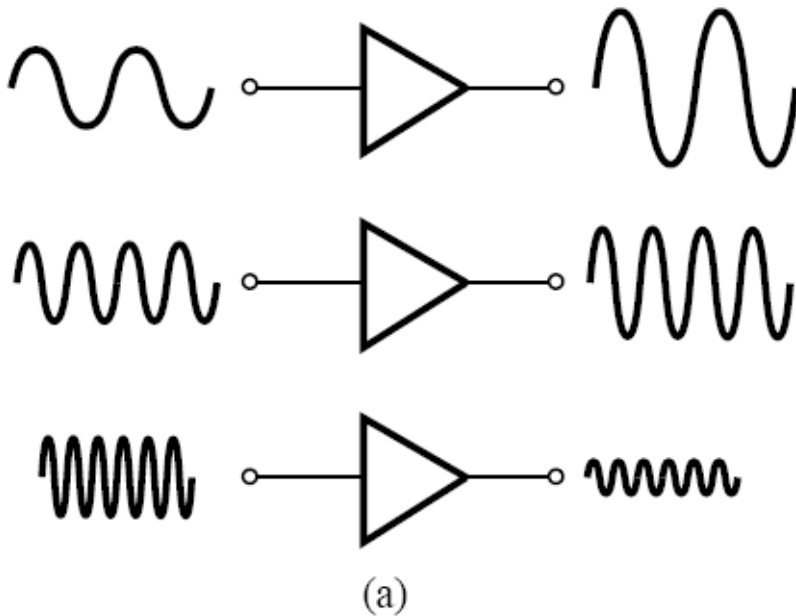

(a) Conceptual test of frequency response, (b) gain roll-off with frequency [2].



**As frequency of operation increases, the gain of amplifier decreases.**

# Bode Plot

$$H(s) = A_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right) \dots}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \dots}$$

- A zero,  $\omega_{zj} \Rightarrow$  the Bode magnitude rises with a slope of +20dB/dec.
- A pole,  $\omega_{pj}$ , the Bode magnitude falls with a slope of -20dB/dec

## Example – simple low pass filter

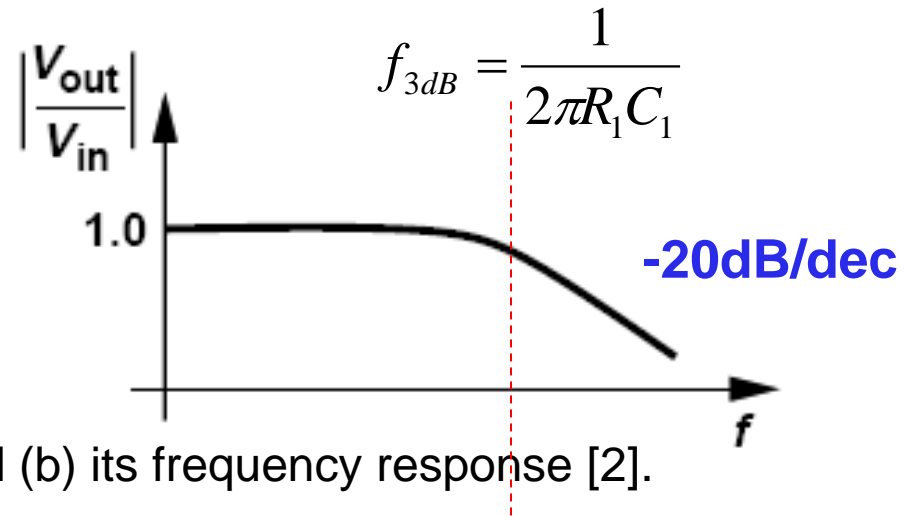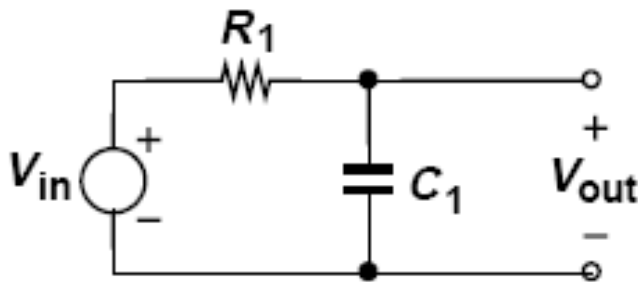


(a) Simple low-pass filter, and (b) its frequency response [2].

$$H(s) = \frac{1}{(1 + sR_1C_1)}$$
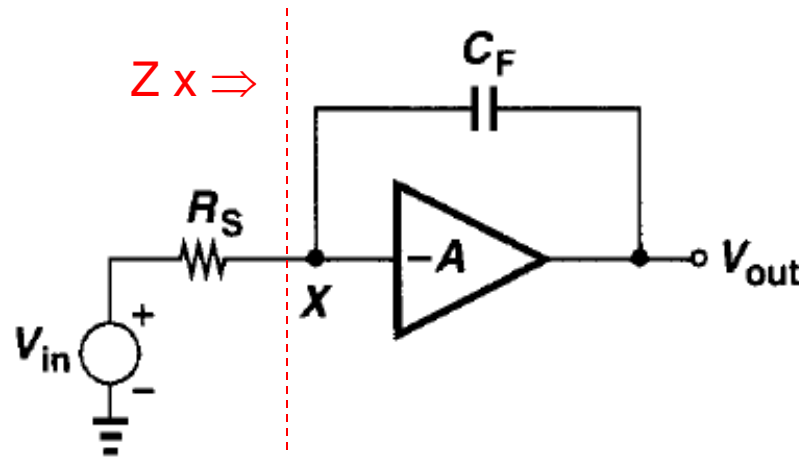
## Association of Poles with Nodes – ex. 3

Let's calculate the pole associated with node X [1]:




$$Z_X = \frac{V_X}{I_X} = \frac{V_X}{(V_X - V_{out})sC_F} = \frac{V_X}{(V_X + AV_X)sC_F} = \frac{1}{(1+A)sC_F}$$

**Effective capacitance to ground from node X:**


$$C_X = (1+A)C_F$$

Pole associated with node X:  $p_X = -\frac{1}{(1+A)C_F R_S}$

# MOS Intrinsic Capacitances

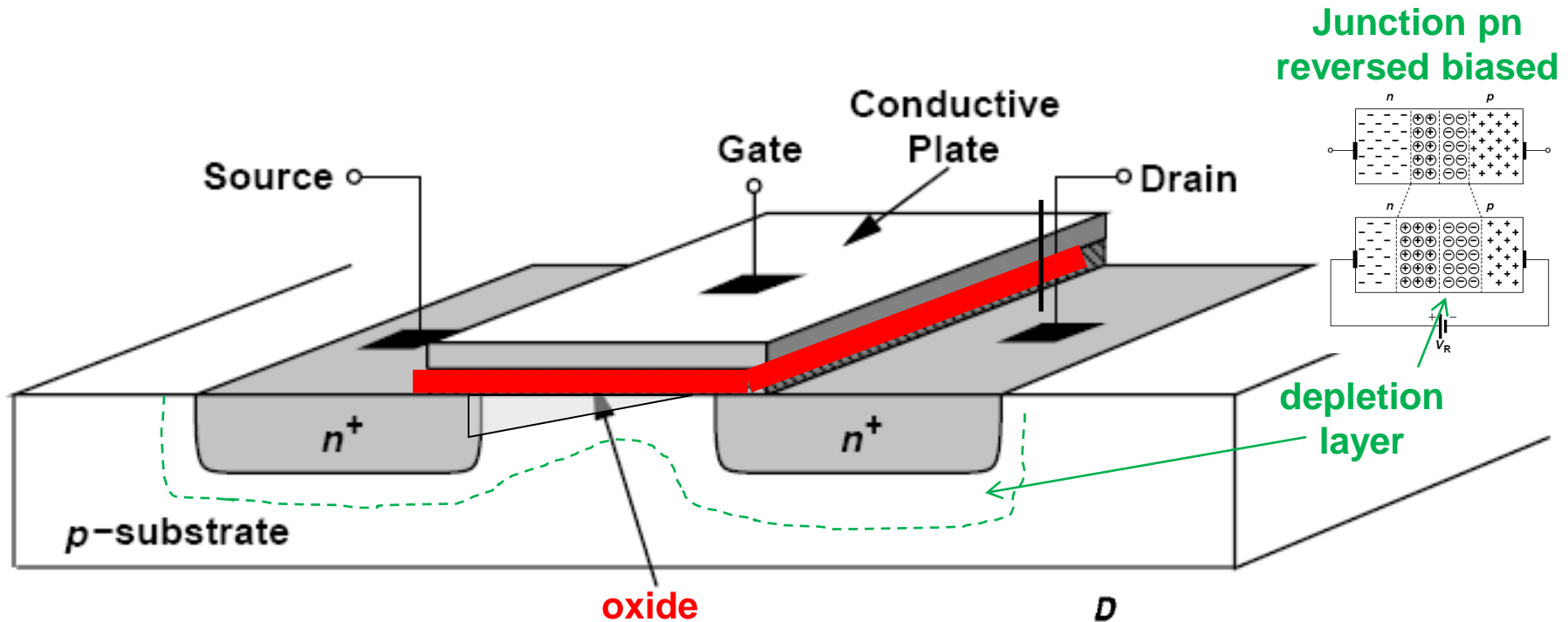


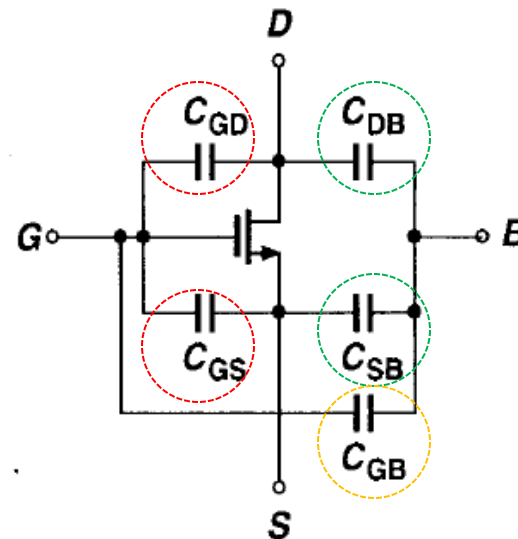For a MOS, there exist **oxide capacitance** from gate to channel, **junction capacitances** from source/drain to substrate, and overlap capacitance from gate to source/drain.


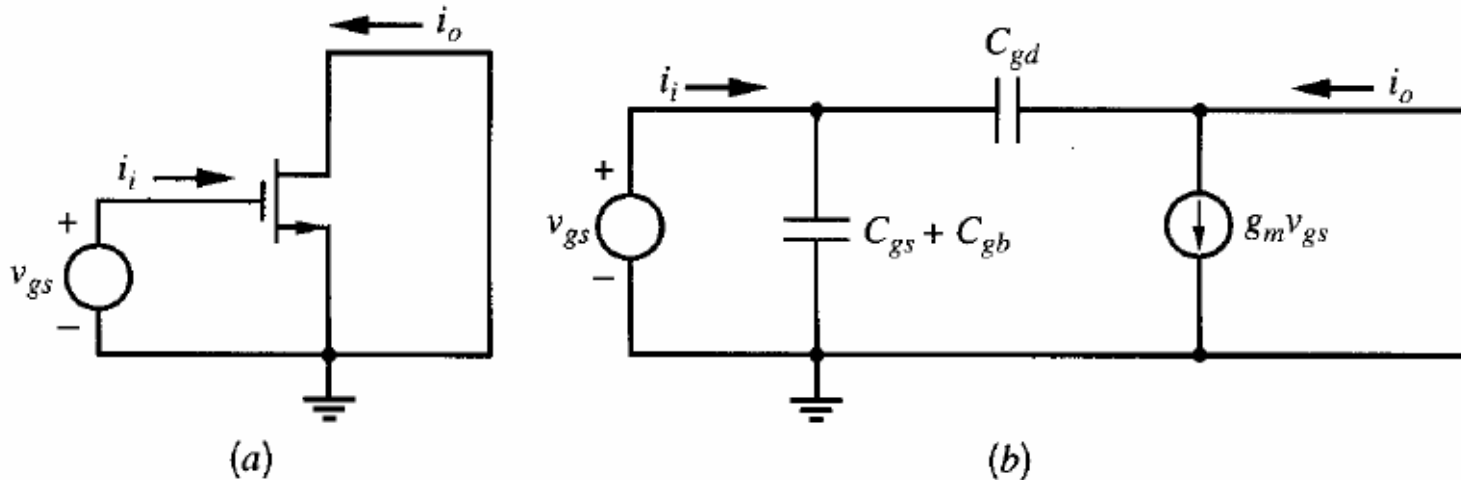
# MOS transistor frequency response

Transition frequency  $f_T$  is defined as the frequency where the magnitude of the short-circuit, common source current gain falls to unity.



Circuit for calculating  $f_T$ : a) AC schematic, b) small signal equivalent [3].

Small signal input current

$$i_i = s(C_{GS} + C_{GB} + C_{GD})v_{gs}$$

$$\frac{i_o}{i_i} \approx \frac{g_m}{s(C_{GS} + C_{GB} + C_{GD})}$$


If the current fed forward through CGD is neglected

$$i_o \approx g_m v_{gs}$$

$$f_T \approx \frac{g_m}{2\pi(C_{GS} + C_{GB} + C_{GD})} \approx \frac{g_m}{2\pi C_{GS}}$$


# Frequency response of CS stage

## Miller approximation [3]

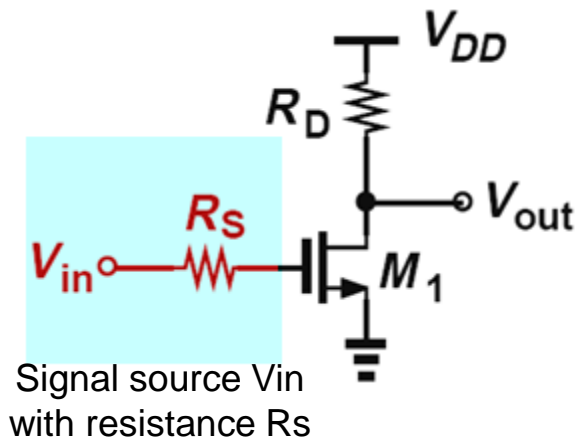

$$C_M = (1 - A_{v0})C_{GD}$$

LOW FREQUENCY

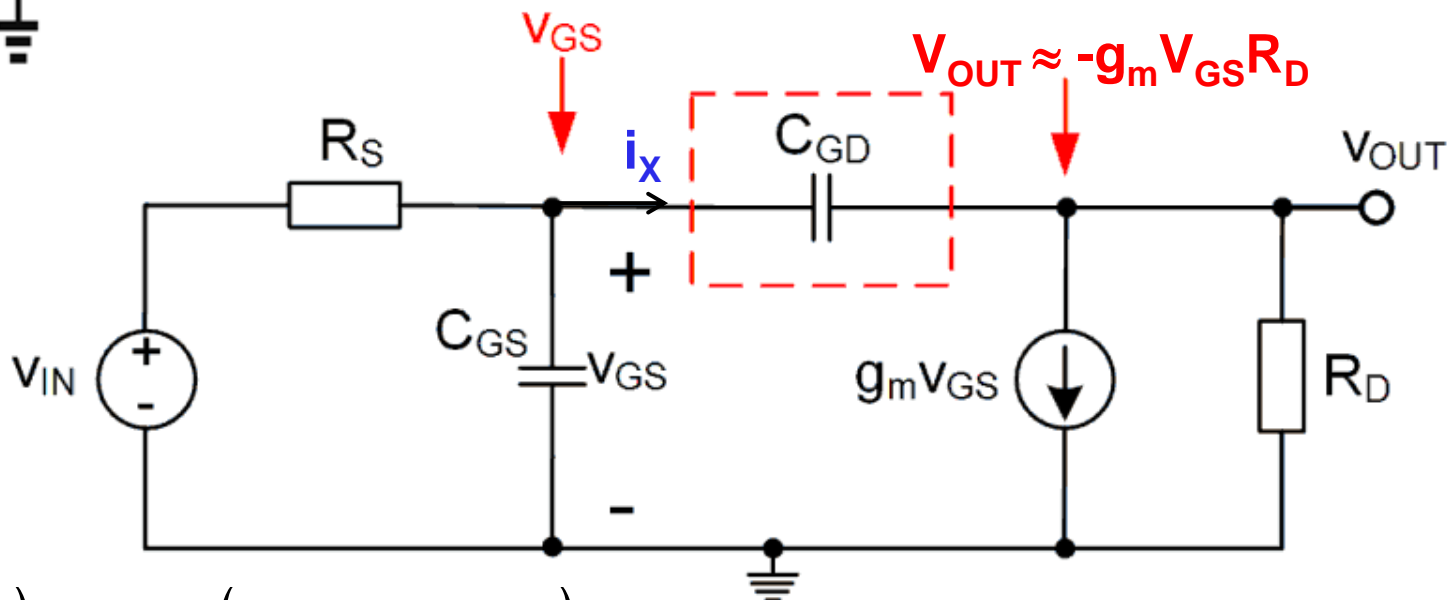


$$\frac{i_x}{v_{gs}} = \frac{(v_{gs} - v_{out})sC_{GD}}{v_{gs}} \approx \frac{(v_{gs} + g_m v_{gs} R_D)sC_{GD}}{v_{gs}} = (1 + g_m R_D)sC_{GD}$$

$$C_M = (1 + g_m R_D)C_{GD}$$



# Frequency response of CS stage

## Miller approximation [3]

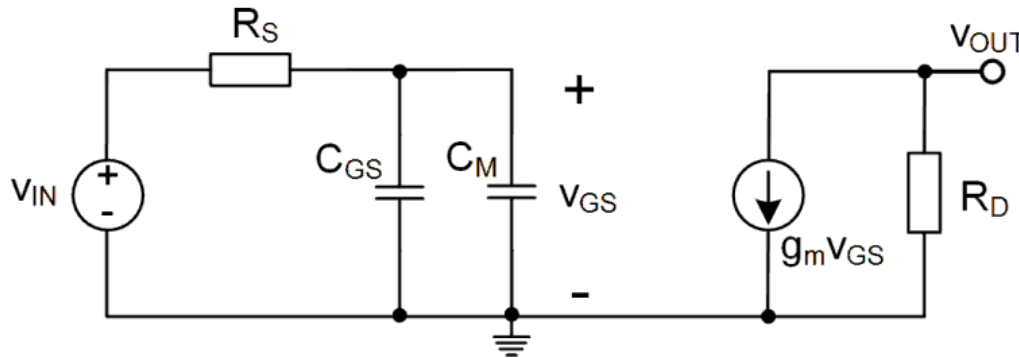

$$C_M = (1 + g_m R_D) C_{GD}$$

Input impedance

$$1/Z_{in} = s \left[ C_{GS} + \underbrace{(1 + g_m R_D) C_{GD}}_{C'_M} \right]$$

Transfer function


$$v_{out} = -g_m R_D v_{gs} = -g_m R_D \frac{\frac{1}{sC'_M}}{\frac{1}{sC'_M} + R_S} v_{in} = -g_m R_D \frac{1}{1 + sC'_M R_S} v_{in}$$

Dominant pole:

$$p_1 = -\frac{1}{R_S (C_{GS} + (1 + g_m R_D) C_{GD})}$$

# Frequency CS stage

## Exact gain expression [3]

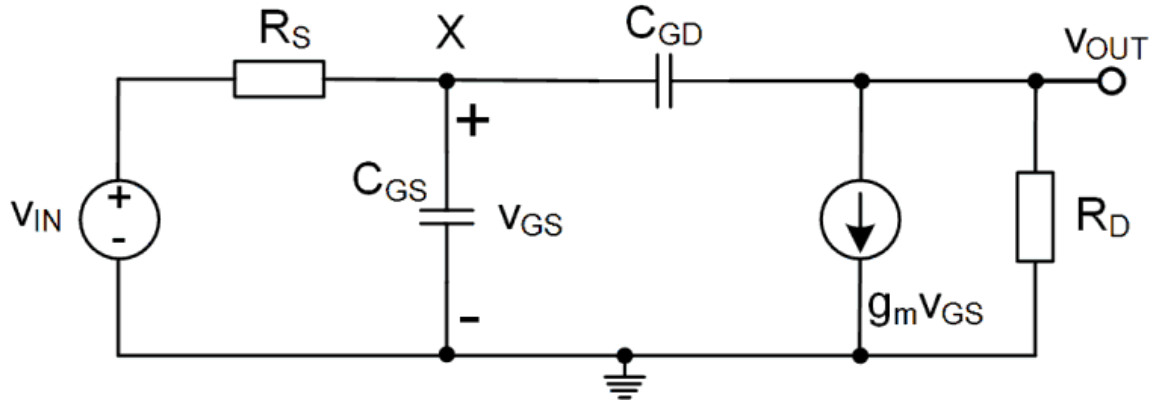

KCL for node X:

$$\frac{v_{in} - v_{gs}}{R_S} = v_{gs} s C_{GS} + (v_{gs} - v_{out}) s C_{GD} \quad \Rightarrow \quad v_{in} = v_{gs} [1 + s(C_{GS} + C_{GD})R_S] - v_{out} s C_{GD} R_S$$

KCL for node OUT:

$$(v_{gs} - v_{out}) s C_{GD} = g_m v_{gs} + \frac{v_{out}}{R_D} \quad \Rightarrow \quad v_{gs} = \frac{1 + s C_{GD} R_D}{s C_{GD} R_D - g_m R_D} v_{out}$$

Transfer function:

$$\frac{v_{out}}{v_{in}} = \frac{-g_m R_D (1 - s C_{GD} / g_m)}{s^2 C_{GD} C_{GS} R_D R_S + s \{ R_S [C_{GS} + (1 + g_m R_D) C_{GD}] + C_{GD} R_D \} + 1}$$

Positive real zero and two poles

# Frequency CS stage

## Exact gain expression [3]

If the poles are  $p_1$  and  $p_2$   
we can write the dominator

$$D(s) = \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) = 1 - s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}$$

If the poles are real and  
widely separated  $|p_1| \ll |p_2|$

$$D(s) \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$$

Transfer function:

$$\frac{v_{out}}{v_{in}} = \frac{-g_m R_D (1 - s C_{GD} / g_m)}{s^2 C_{GD} C_{GS} R_D R_S + s \{R_S [C_{GS} + (1 + g_m R_D) C_{GD}] + C_{GD} R_D\} + 1}$$

Poles:

$$p_1 = \frac{-1}{\underbrace{R_S [C_{GS} + (1 + g_m R_D) C_{GD}] + C_{GD} R_D}_{\text{Miller approx.}}}$$

Miller approx.


$$p_2 = - \left( \frac{1}{R_D C_{GD}} + \frac{1}{R_D C_{GS}} + \frac{1}{R_S C_{GS}} + \underbrace{\frac{g_m}{C_{GS}}}_{\text{Transfer frequency (very high)}} \right)$$

Transfer frequency  
(very high)


Positive real zero

$$z = \frac{g_m}{C_{GD}}$$

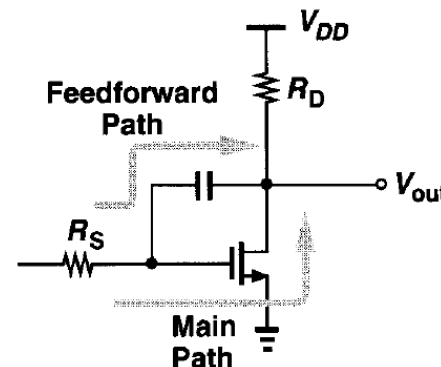
Located in the right half plane  
introduces **stability** issues in  
feedback amplifier)



# Frequency CS stage - example


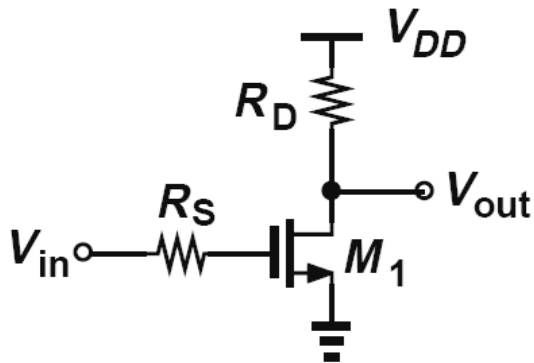


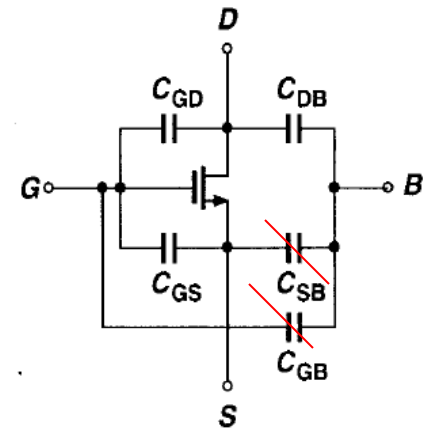Example:  
 $R_S=200\Omega$ ,  $R_D=2k\Omega$ ,  
 $g_m=(150\Omega)^{-1}$ ,  $\lambda=0$   
 $C_{GS}=250fF$ ,  $C_{GD}=80fF$ ,  
 $C_{DB}=100fF$



	Miller's approx.	Calculation with $ p_1  \ll  p_2 $	Calculation with $ p_1  \ll  p_2 $ and CDB	Exact calculation and CDB
$f_{p1}$	568 MHz	362 MHz	249 MHz	264 MHz
$f_{p2}$	-	8.73 GHz	4.79 GHz	4.53 GHz
$f_{zero}$	-	13.2 GHz	13.2 GHz	13.2 GHz

## Frequency CS stage - conclusions

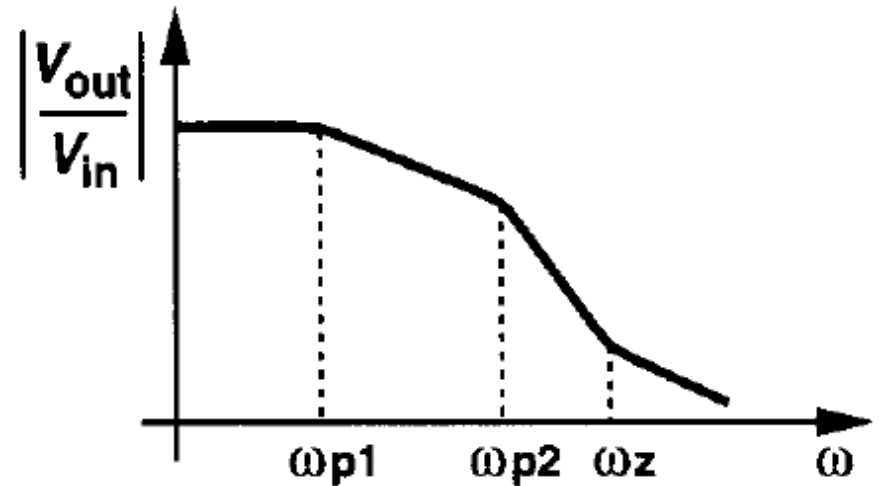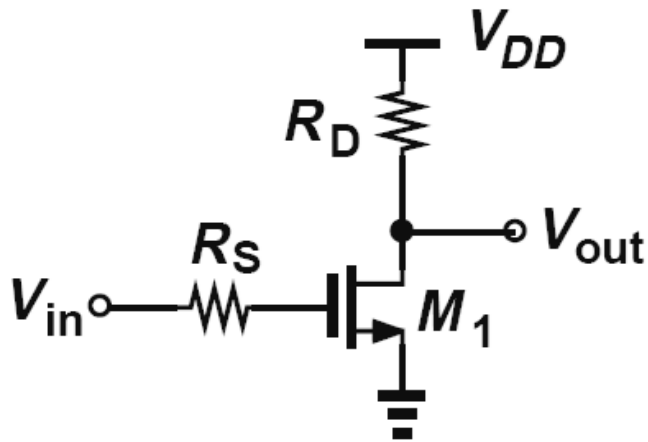


- **Miller's approx:** fast and very effective for dominant pole
- **Exact calculaton:** positive zero and two widely separted poles
- **Input impedance:** capacitive - Miller multiplication (for higher frequency see [1])



**ADDITIONAL SLIDES**
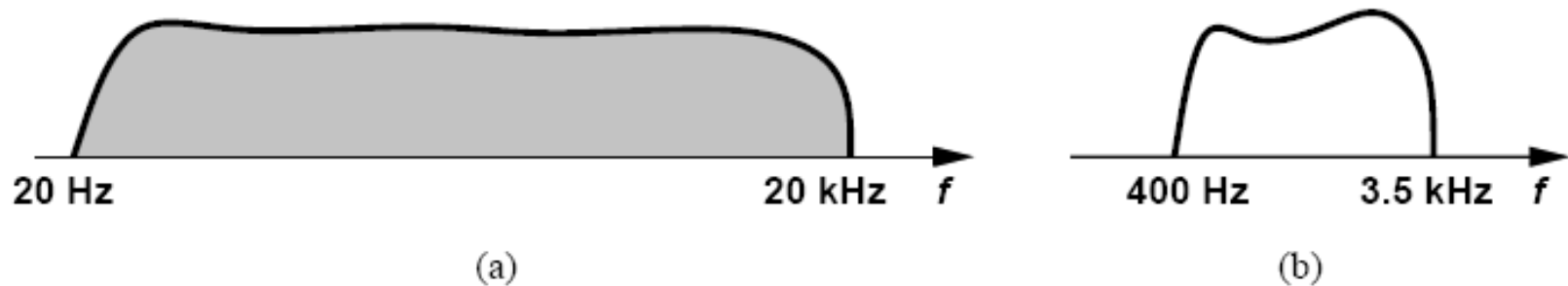
## Example: Human Voice

Why people's voice over the phone sounds different from their voice in face-to-face conversation?




(a) Natural voice, (b) telephone system [2].

Natural human voice spans a frequency range from 20 Hz to 20 kHz, however conventional telephone system passes frequencies from 400Hz to 3.5 kHz.

## Association of Poles with Nodes – ex. 1

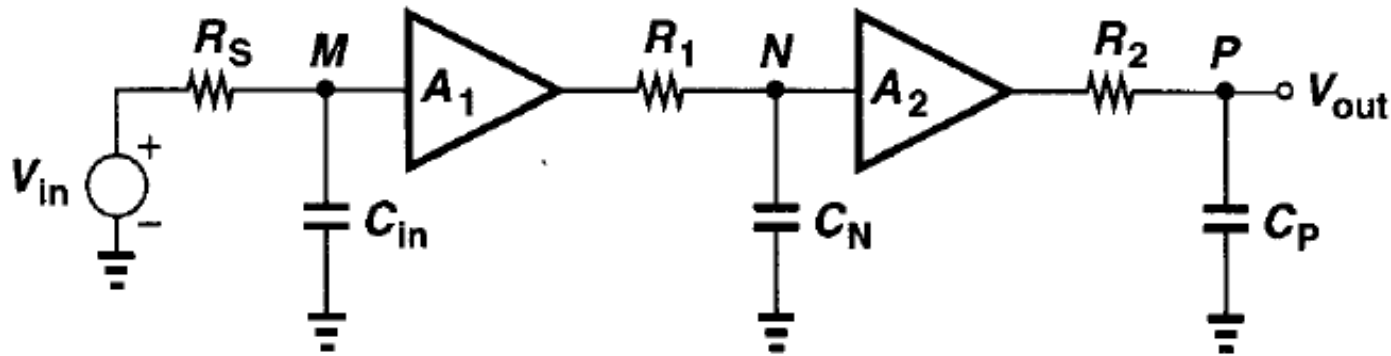Example - a cascade amplifiers:  $A_1$  and  $A_2$  are ideal voltage amplifiers,  $R_s$  is source resistance,  $R_1$  and  $R_2$  model the output resistance of each stage,  $C_{in}$  and  $C_N$  represents the input capacitance of each stage and  $C_p$  is the load capacitance.



Cascade of amplifiers [1].


$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + R_s C_{in} s} \cdot \frac{A_2}{1 + R_1 C_N s} \cdot \frac{1}{1 + R_2 C_p s}$$

**Three poles – each of which is determined by the total capacitance seen from each node to ground multiplied by the total resistance seen at the node to ground**



## Association of Poles with Nodes – ex. 2

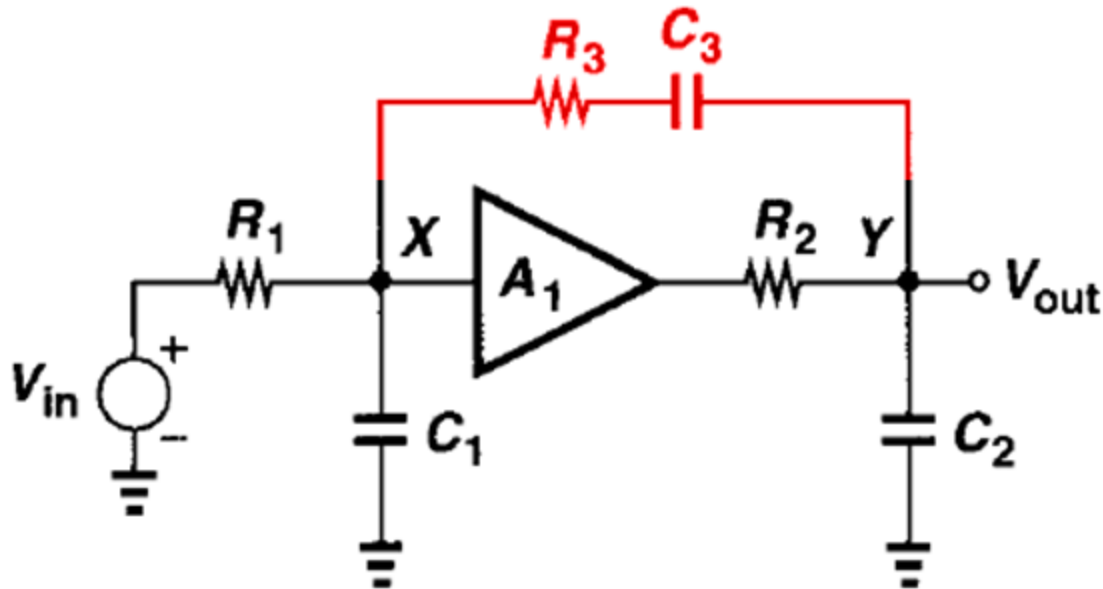Example of interaction between two nodes [1]:



The location of the poles is difficult to calculate because  $R_3$  and  $C_3$  create interaction between X and Y.

# Miller's Theorem

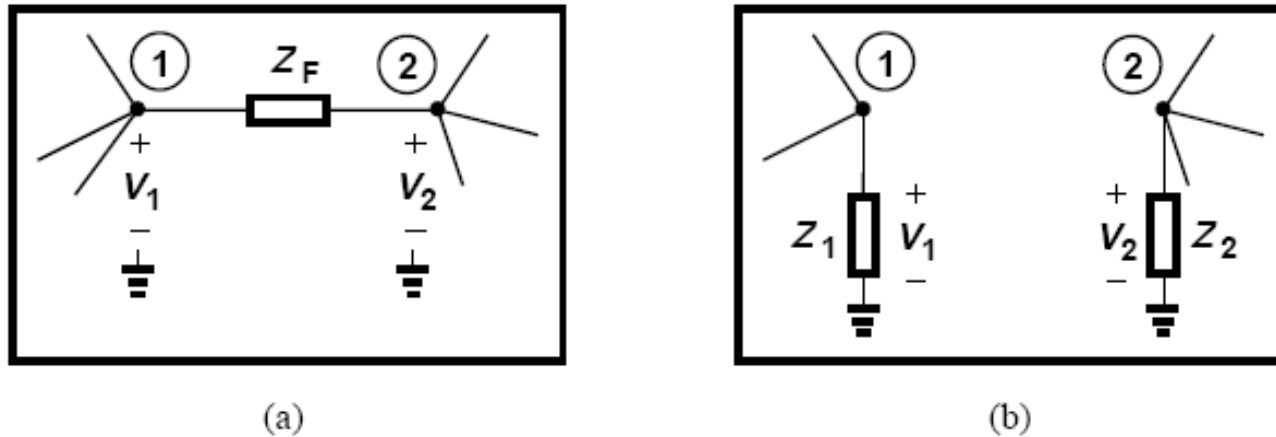


Fig. 1 (a) General circuit including a floating impedance, (b) equivalent of (a) as obtained from Miller's theorem [2].


If the circuit of Fig. 1(a) can be converted to that of Fig. 1(b) , then

$$Z_1 = \frac{Z_F}{1 - A_v}$$


$$Z_2 = \frac{Z_F}{1 - 1/A_v}$$

where  $A_v = \frac{V_Y}{V_X}$

## Miller Multiplication – example

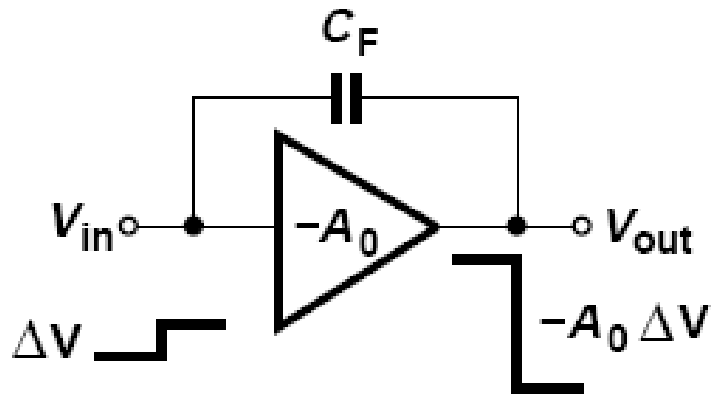

(a)


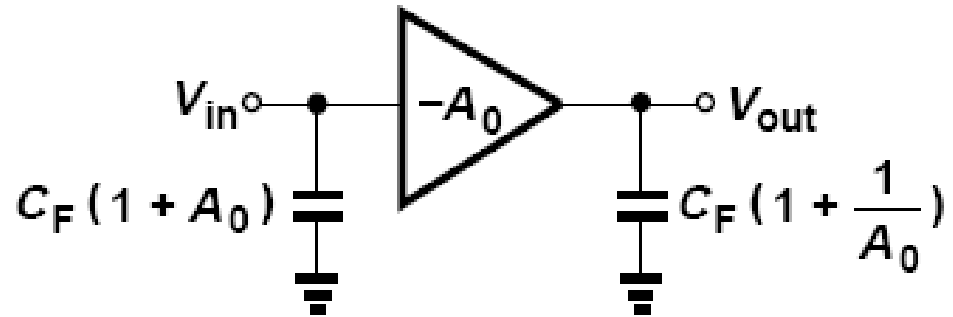


(b)

(a) Inverting circuit with floating capacitor, (b) equivalent circuit as obtained from Miller's theorem [2].

With Miller's theorem, we can separate the floating capacitor. However, the input capacitor is larger than the original floating capacitor. **We call this Miller multiplication.**

# Miller's Approximation [4]

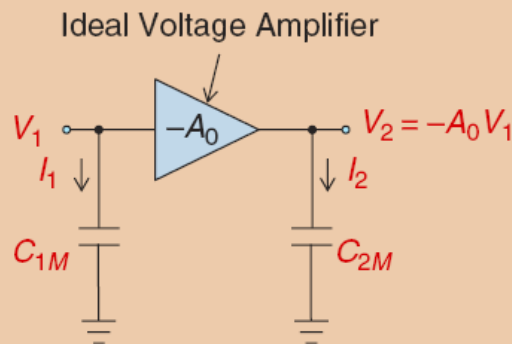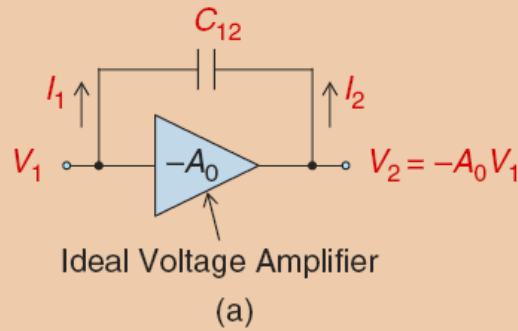

$$C_{1M} = C_{12} (1 + A_0)$$

$$C_{2M} = C_{12} \left(1 + \frac{1}{A_0}\right)$$

1. How to apply Miller's theorem when its gain is frequency dependent (i.e., not constant)?

$$A_V(j\omega) = \frac{-A_0}{1 + \frac{j\omega}{\omega_p}} \quad \longrightarrow \quad C_{1M} = C_{12} \left( 1 + \frac{A_0}{1 + \frac{j\omega}{\omega_p}} \right)$$

**$C_{1M}$  is frequency dependent !**


2. How to apply Miller's theorem when the amplifier is nonideal (e.g., has a finite output impedance)?

see: [4] Ali Sheikholeslami: Miller's Approximation. IEEE SSC Magazine, Fall 2015, p.7-8,13

**In summary**, Miller's approximation uses the **dc gain of the amplifier to provide a relatively accurate estimation of its dominant pole** (i.e., the circuit bandwidth). This approximation, however, becomes inaccurate when determining the second pole of the amplifier; other intuitive methods exist for this purpose [4].



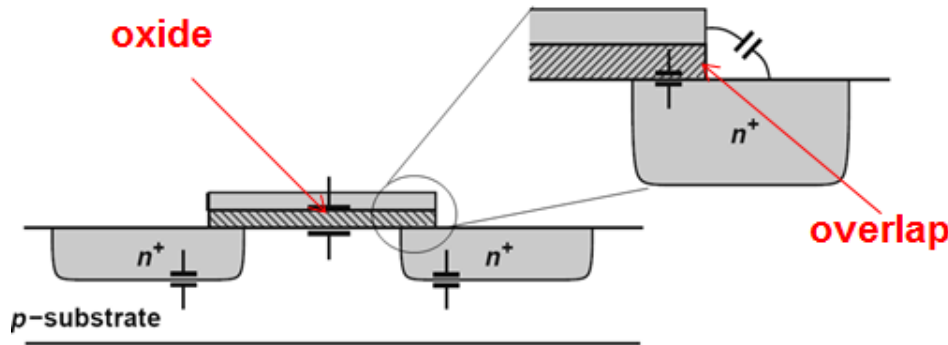
# Variation of CGS and CGD versus VGS [1].

Two components of CGS and CGD: **channel** + **overlap**



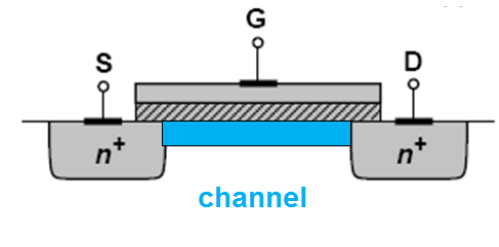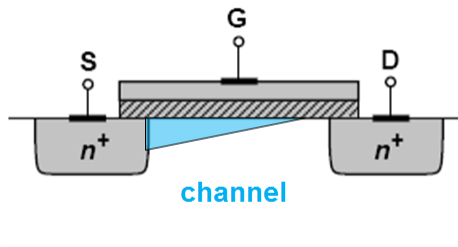
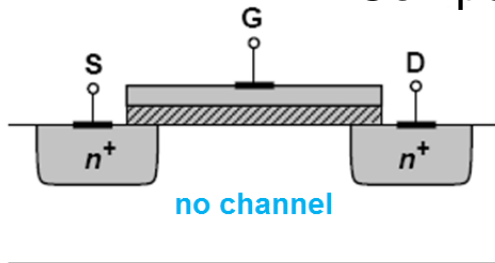
Example - CMOS 130nm  
 $t_{ox} = 2.7 \text{ nm}$   
 $C_{ox} = 12.8 \text{ fF}/\mu\text{m}^2$   
 $C_{ov} = 0.35 \text{ fF}/\mu\text{m}$

Component gate-channel depends on  $V_{GS}$




$$C_{GS} = f(V_{GS})$$

$$C_{GD} = f(V_{GS})$$

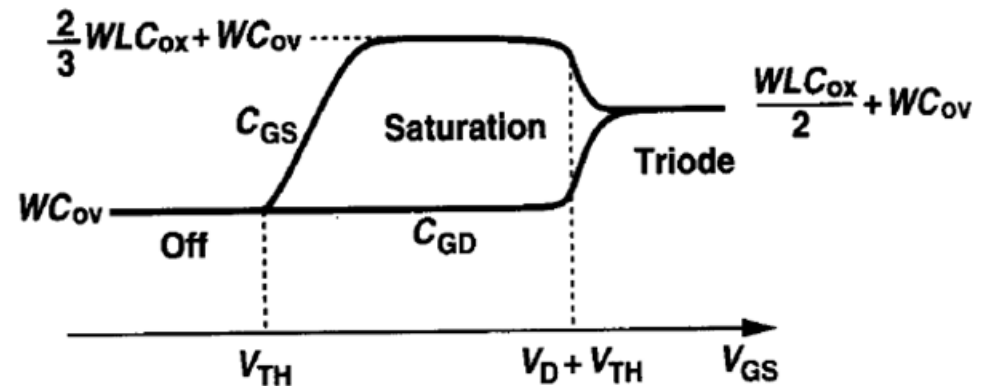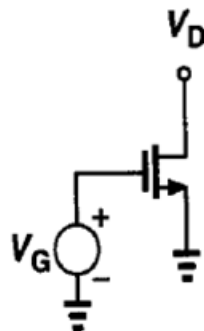

# Complete MOS small-signal model [1]

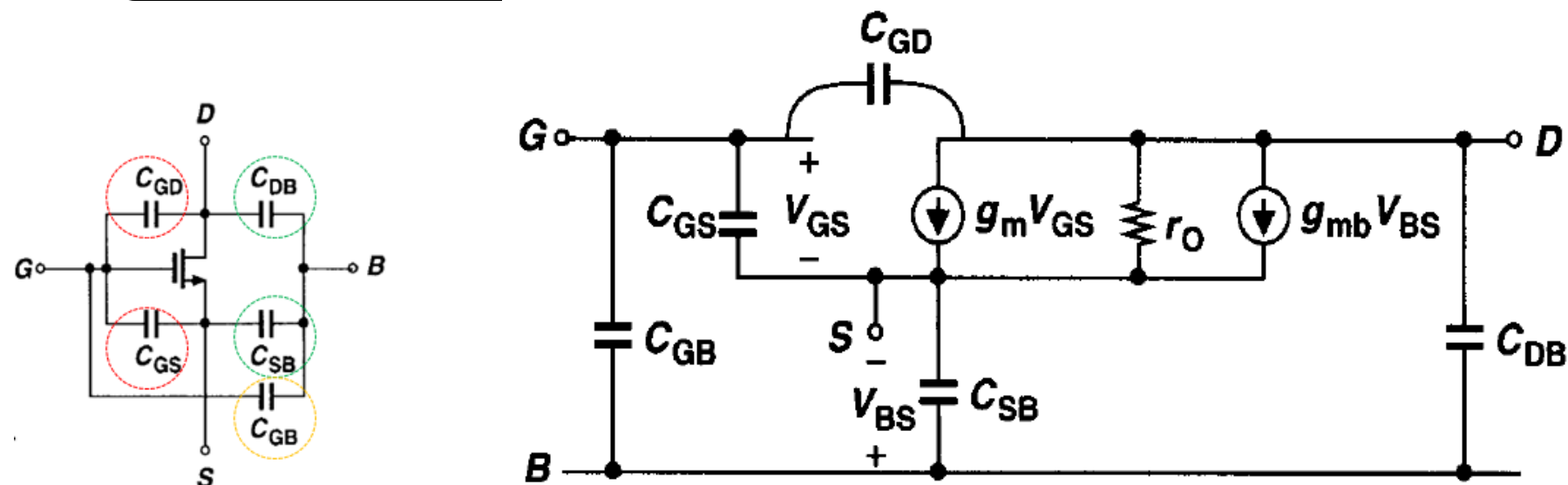

Technology	Drain current ( $V_{GS}=V_{DS}$ )	W/L [ $\mu\text{m}/\mu\text{m}$ ]	$C_{GS}$ [F]	$C_{GD}$ [F]	$C_{SB}$ [F]	$C_{DB}$ [F]	$C_{GB}$ [F]
130 nm	100 $\mu\text{A}$	100 / 0.2	55 f	44 f	2.1 f	103 f	32 f
	10 $\mu\text{A}$		45 f	44 f	0.16 f	106 f	25 f
45 nm	100 $\mu\text{A}$	100 / 0.2	77 f	15 f	8.9 f	0.048 f	19 f
	10 $\mu\text{A}$		34 f	15 f	2.9 f	0.026 f	25 f
130 nm	10 $\mu\text{A}$	0.15 / 0.13 (min)	0.181 f	0.071 f	0.637 f	0.540 f	0.008 f
	1 $\mu\text{A}$		0.103 f	0.072 f	0.627 f	0.565 f	0.018 f
45 nm	10 $\mu\text{A}$	0.12 / 0.04 (min)	0.042 f	0.002 f	-	-	-
	1 $\mu\text{A}$		0.028 f	0.019 f	-	-	-

# Maximum $f_T$ versus channel length $L$ [5]

$$C_{GS} = \frac{2}{3} W L C_{ox} \quad g_m = 2K' \frac{W}{L} (V_{GS} - V_T) \quad K' = \frac{\mu C_{ox}}{2n}$$

$$f_T = \frac{g_m}{2\pi C_{GS}} = \frac{1}{2\pi} \frac{3}{2n} \frac{\mu}{L^2} (V_{GS} - V_T) \quad \text{or} \quad \approx \frac{V_{sat}}{2\pi L}$$


W. Sansen [5] uses the formula for drain current:

$$I_{DS} = \frac{\mu C_{ox}}{2n} \frac{W}{L} (V_{GS} - V_T)^2$$

$$n = 1 + \frac{C_D}{C_{ox}} \approx 1.2 - 1.5$$

This frequency is proportional to  $V_{GS} - V_T$  and inversely proportional to  $L^2$ . Decreasing the channel length allows an higher frequency performance. In velocity saturation however, the time that the electrons need to cross the channel length is  $L/v_{sat}$ . The frequency  $f_T$  in velocity saturation is, to put it simply  $v_{sat}/2\pi L$ . This is the highest frequency that can be obtained with a MOS transistor.

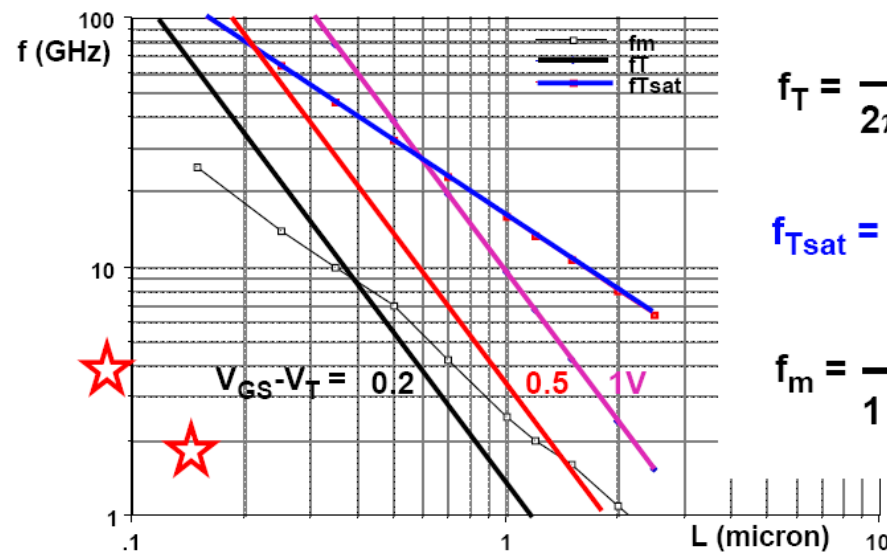1. For technology with  $L \approx 100\text{nm}$   $f_T$  of 100 GHz is available.
2. Experimental upper frequencies of VCO and LNA marked as  $f_m$  is about 1/5 of  $f_T$ .
3. Clock frequency of processors is about 1/100 of  $f_T$ .



Processors

$$f_T = \frac{\mu}{2\pi L^2} \underbrace{(V_{GS} - V_T)}_{0.2 \dots 1 \text{ V}}$$

$$f_{Tsat} = \frac{V_{sat}}{2\pi L}$$

$$f_m = \frac{f_T}{1 + \alpha_{BD}} \quad \alpha_{BD} \approx \frac{C_{BD}}{C_{ox}}$$